

REC FPGA Seminar IAP 1998

Session 3:

Advanced Design Techniques, Optimizations, and Tricks

Outline

- Focus on Xilinx 4000E-style FPGA (one of the most common FPGAs)
- Thinking FPGA
- Black box optimizations
- Counter design
- Distributed arithmetic
- One-hot state machines
- Miscellaneous tricks

Thinking FPGA

- When starting a design, consider the implementation technology
- Architect your design to fit into an FPGA
 - memory granularity (16x1, 16x2, 32x1)
 - 4 or 5 input logic functions / 4 + 4 and 2-1 mux
 - fewer inputs per logic function is wasteful
 - more inputs is slower
 - routing limitations
 - limited number of tristate buffers and longlines
 - limited number of clock buffers
 - I/O cell features
 - flip flops in I/O cells
 - special delays and slew rate control

“Black Box” Optimization

- Most basic of FPGA design optimizations
 - Essentially performing manual hardware mapping
- Procedure:
 - break down design into combinational logic black boxes
 - inputs and outputs with stuff inbetween
 - arbitrarily complex logic inside the box, but CLB doesn't care since it is a LUT anyways
 - adjust the “level” of black-boxing until you have mostly 4 or 5 input functions or 4+4 input and 2-1 mux functions


“Black Box” Example

- ALU
 - implements a 32-bit wide 2-input AND, OR, XOR, pass-through
- Example worked through on chalkboard
 - obvious implementation
 - 3 32-bit wide 2-input devices feeding into a mux or a tri-state bus
 - optimized implementation
 - 32 4-input devices: 66% or more savings in area; roughly 30-50% speed increase

Counter Design


- Counters have many design options depending upon the application
 - basic ripple counter
 - ripple-carry
 - lookahead-carry
 - Johnson (mobius)
 - linear feedback shift register (LFSR)

Ripple Counter

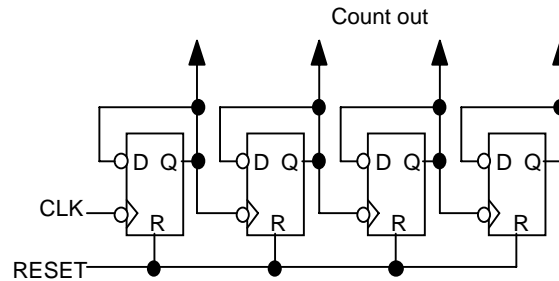

- Ripple carry counter is not recommended in FPGA designs due to their asynchronous nature
- However, ripple carry counters are very efficient in terms of area
- $k \cdot O(n)$ delay growth with the number of bits, k is large (poor performance)
- Max counting states is 2^N

Ripple-Carry Counter

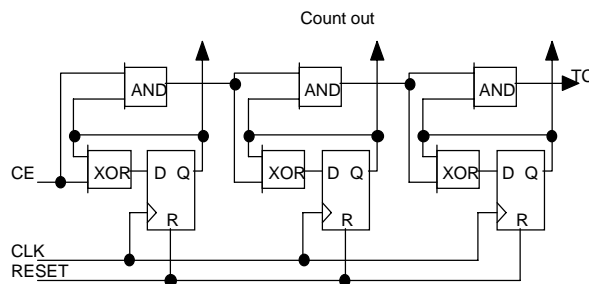


- Synchronous design
- $k \cdot O(n)$ delay growth with n bits, k small
- this is the basic counter provided in Xilinx libraries
- good area efficiency
- Max counting states is 2^N
- Loads or sync clears come for free in terms of area and speed

Carry-Lookahead counter


- Like ripple-carry but carry input to n^{th} counter element is computed using a full sum-of-products of the previous $(n-1)$ bits counter state
- Can have near $O(1)$ delay growth up to a few bits
- Good performance
- Requires a lot of gates
- Combinations of carry-lookahead and ripple-carry can be used to get the best of both worlds
- Max counting states is 2^N

Johnson or Mobius Counter

 

- $O(1)$ delay growth for most applications
- Well-suited for clock division or count-limit only applications
- Non-binary counter
- Counts to $2 * n$, where n is the number of flip flops
- Excellent area and speed characteristics
- Near toggle-rate speeds

LFSR Counters

 

- $O(1)$ delay growth for most applications
- non-binary counter
- $2^N - 1$ states in a pseudorandom sequence
- excellent area and speed characteristics
- near toggle-rate speeds
- ideal for applications where count sequence is irrelevant (FIFO, timers)

LFSR application

- FIFO application
 - Count sequence doesn't matter
 - just need to address unique memory locations
 - last count value and half-full count values can be predetermined and logic created to detect these conditions
 - Saves area, increases performance
 - no carry look-ahead structures, $O(1)$ delay growth with increasing FIFO depth

Distributed Arithmetic

- Parallel multipliers are expensive to implement in FPGAs
 - requires very wide logic functions or the use of carry-chains
 - hardware and delay growth $O(n^2)$
- Distributed arithmetic serializes multiplies using partial products
 - partial products can be computed in parallel
 - serialized multiplies fit well into FPGA architectures
 - can achieve same throughput as parallel multiplier silicon macros but with longer latency

Distributed Arithmetic

- DA takes advantage of associative and commutative properties of addition

Digit nomenclature: $A = a_n a_{n-1} \dots a_2 a_1$

In base 10:

$$A * B = P_n + P_{n-1} + \dots P_2 + P_1 \text{ where } P_n = A * b_n * 10^{n-1}$$

$$\text{So } 42 * 121 = 42 * 1 * 100 + 42 * 2 * 10 + 42 * 1 * 1$$

In base 2:

$$A * B = P_n + P_{n-1} + \dots P_2 + P_1 \text{ where } P_n = A * b_n * 2^{n-1}$$

$$\text{So } 101 * 1101 = (101 * 1) \lll 3 + (101 * 1) \lll 2 + (101 * 0) \lll 1 + (101 * 1) \lll 0$$

multiply operator breaks down to AND operation in one-digit binary; be careful of sign extensions for signed numbers!

Distributed Arithmetic


- Looking at the relation

$$101 * 1101 = \boxed{(101 * 1) \lll 3} + \boxed{(101 * 1) \lll 2} + \boxed{(101 * 0) \lll 1} + \boxed{(101 * 1) \lll 0}$$

- One sees a basic functional unit- the scaling multiply. This, combined with an accumulator and bit-serial input stream (via “time skew buffer”), is the essence of the DA multiplier
- Note that the DA implementation discussed here works best for constant * variable expressions, which is ideally suited for applications such as convolutions and DSP filters
 - replace the $(A * b_n)$ multiply kernel by a lookup-table instead of several AND gates
 - LUTs in some architectures are more efficient than AND gates
- Time to compute = number of bits in input * time to do scaling multiply

Distributed Arithmetic

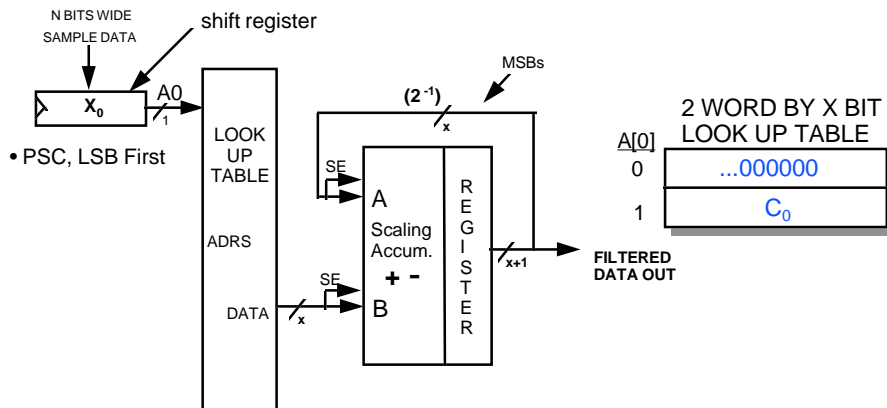- Implementation for variable * C_0 ; computes result in N clock cycles
 - diagram courtesy Xilinx



Distributed Arithmetic

- so what?
 - the real power of DA comes in when you try to do multiple-tap FIR filters

$$y[n] = \sum x[k] * h[n - k]$$

$$y[1] = x[0] * h[1] + x[1] * h[0]$$

Example: $101 * 011 + 110 * 100$

$$= (101 * 0) \lll 2 + (101 * 1) \lll 1 + (101 * 1) \lll 0 + (110 * 1) \lll 2 + (110 * 0) \lll 1 + (110 * 0) \lll 0$$

$$= \boxed{(101 * 0) + (110 * 1) \lll 2} +$$

$$\boxed{(101 * 1) + (110 * 0) \lll 1} +$$

$$\boxed{(101 * 1) + (110 * 0) \lll 0}$$

These boxes are about as complex as the boxes used in the one-tap case!

Distributed Arithmetic for a 3-Tap Filter


X	X	X	
-2 ³ 2 ² 2 ¹ 2 ⁰	-2 ³ 2 ² 2 ¹ 2 ⁰	-2 ³ 2 ² 2 ¹ 2 ⁰	
1 0 0 1 (-7)	0 1 1 0 (6)	0 0 1 0 (2)	
0 1 1 1 (7)	0 1 0 1 (5)	0 1 1 1 (7)	
(1 0 0 1 +	0 1 1 0 +	0 0 1 0)	→ ← 0 0 0 1
(1 0 0 1 +	0 0 0 0 +	0 0 1 0)	→ ← 1 0 1 1
(1 0 0 1 +	0 1 1 0 +	0 0 1 0)	→ ← 0 0 0 1
(0 0 0 0 +	0 0 0 0 +	0 0 0 0)	→ ← 0 0 0 0
1 1 0 0 1 1 1 1 (-49)	0 0 0 1 1 1 1 0 (30)	1 1 0 0 1 1 1 1 (14)	= 1 1 1 1 1 0 1 1 (-5)

- Partial Products of equal weight are added together before being summed to next higher partial product weight.

← = Sign Extension

(slide courtesy Xilinx)


Distributed Arithmetic

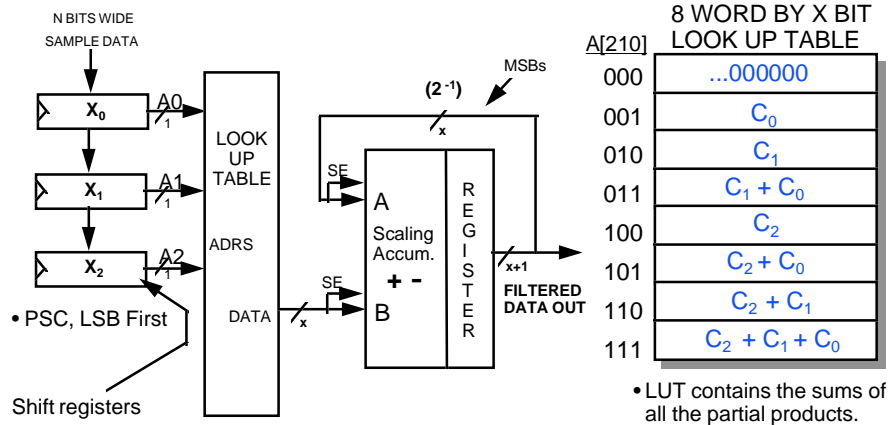

(slide courtesy Xilinx)

Distributed Arithmetic

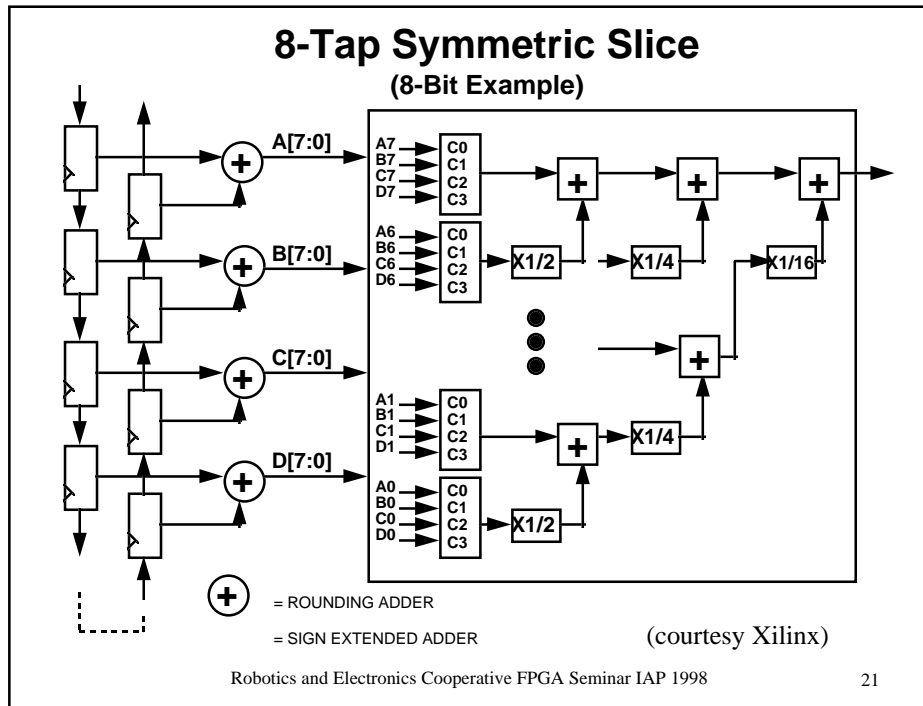- $k O(2^n) + j O(1)$, k is relatively small (for area)
- very close to $O(1)$ performance scaling
- DA can be parallelized and pipelined to gain even more performance
 - Each bit can have its own LUT and adder
 - All bits computed in parallel
 - One result per clock cycle max throughput




- ## Distributed Arithmetic
- Performance
 - Serial Distributed Arithmetic (SDA), 10-tap FIR
 - 7.8 Msamp/s for 8 bit samples @ 42 CLBs
 - 4.1 Msamp/s for 16 bit samples @ 50 CLBs
 - old numbers; probably 50% faster now
 - Parallel Distributed Arithmetic (PDA), 8-tap FIR
 - 50-70 Msamp/s for 8 bit samples @ 122 CLBs
 - pipelined, hand-optimized
 - For reference, the XC4008E has 324 CLBs (18 x 18 array)
- Robotics and Electronics Cooperative FPGA Seminar IAP 1998 22

One-Hot State Machines

- Conventional state machines use $\log_2(\text{states})$ bits to implement function
 - output is decoded from state number
 - next state is a combinational function of states
 - state transition rate limited by state number decoding and next state logic delays
- One-hot state machines use as many bits as there are states to implement function
 - only one flip flop storing “1” at any time
 - output is decoded as an OR of appropriate state FFs
 - state transition rate limited only by next state logic delays, which in many cases is zero

Miscellaneous Tricks

 - Tri-state mux
 - saves on area, especially for wide muxes
 - may have better or worse performance depending on architecture and device characteristics
 - not shown in illustration is decoder for tri-state buffers



Miscellaneous Tricks

- Use IOBs to register inputs
 - gives faster setup/hold times (eliminates routing delays from setup time)
 - introduces additional latency
 - can save on logic array flip flop usage
- Inverters come for free in most architectures
- Use longlines for timing-critical signals
 - use sparingly since this is a precious resource in Xilinx 4K architectures
 - all wires in Altera “Fast Track” architecture are longlines so routes are always “fast”
- Use pipeline stages to improve pin-locked routing in Altera 8K designs
- When you can afford it, pipeline your design
 - latency versus clock speed tradeoff
- Double-wide half-rate logic (area versus speed)